



# Tutorial 3

# Flip-Flops

COMP2120B Computer organization

Kevin Lam (yklam2)

 
# Overview



- A combinational circuit generates outputs base on the current input only.




- A sequential circuit generates outputs base on the current and the past input.



- Past input is usually captured using the previous output.
- Flip-flop is one of the simplest form of sequential circuit, we start with the S-R latch.
 
# Analyzing S-R latch

- The S-R latch and the corresponding truth table.



Input				Output	
S	R	Q	$\bar{Q}$	Q	$\bar{Q}$
0	0	0	0	1	1
0	0	0	1	0	1
0	0	1	0	1	0
0	0	1	1	0	0
0	1	0	0	0	1
0	1	0	1	0	1
0	1	1	0	0	0
0	1	1	1	0	0
1	0	0	0	1	0
1	0	0	1	0	0
1	0	1	0	1	0
1	0	1	1	0	0
1	1	0	0	0	0
1	1	0	1	0	0
1	1	1	0	0	0
1	1	1	1	0	0

## Observation


As output  $Q$  and  $\bar{Q}$  will be served as input immediately,  
The output will be updated again for the highlighted cases.

# Stable state

Input				Output(1)		Output(2)		Output(3)	
$S$	$R$	$Q$	$\bar{Q}$	$Q$	$\bar{Q}$	$Q$	$\bar{Q}$	$Q$	$\bar{Q}$
0	1	1	0	0	0	0	1	0	1

State won't change anymore

- Let's consider one of the case



 


# Unstable state

Input				Output(1)		Output(2)		Output(3)	
$S$	$R$	$Q$	$\bar{Q}$	$Q$	$\bar{Q}$	$Q$	$\bar{Q}$	$Q$	$\bar{Q}$
0	0	0	0	1	1	0	0	1	1

State will never be stable

- Let's consider another case

   

# S-R Latch – stable states

- We can repeat the analysis to find all stable states.
  - The latch is unstable only when  $S$  and  $R$  were set to zero AND when  $Q = \bar{Q}$ .
    - However, this happens only when we set both  $S$  and  $R$  to 1.
  - If we avoid setting both  $S$  and  $R$  to 1, we can always avoid reaching an unstable state.
    - $Q$  and  $\bar{Q}$  are then always complementary.
- The result can then be further summarized.


$S$	$R$	$Q_{n+1}$
0	0	$Q_n$
0	1	0
1	0	1
1	1	-

Input				Output	
$S$	$R$	$Q$	$\bar{Q}$	$Q$	$\bar{Q}$
0	0	0	0	Unstable	
0	0	0	1	0	1
0	0	1	0	1	0
0	0	1	1	Unstable	
0	1	0	0	0	1
0	1	0	1	0	1
0	1	1	0	0	1
0	1	1	1	0	1
1	0	0	0	1	0
1	0	0	1	1	0
1	0	1	0	1	0
1	0	1	1	1	0
1	1	0	0	0	0
1	1	0	1	0	0
1	1	1	0	0	0
1	1	1	1	0	0
 
# Clocked S-R Latch




- To synchronize S-R state with clock pulse, the clock signal is used to control when the input of S and R should be taken.



Only when clock is 1, the 1 in S or R could be sent to the latch


# S-R Flip-flops

 


- **Bistable** device, could be used to store 1 bit of data.
- Built from **clocked latches**.
- Two outputs, which are always the complements of each others. ( $Q$  and  $\overline{Q}$ )
- Two other typical flip-flops are D flip-flop and J-K flip-flop.



# D flip-flop

 


 - Single input (D).
- Also called data flip-flop or delay flip-flop.
- Using a NOT gate, forcing only one of the input for the S-R latch to be 1.




D	$Q_{n+1}$
0	0
1	1

# J-K flip flop

 



 
- Same as S-R flip-flop, except that it allows both inputs to be 1, which will toggle the state.



$J$	$K$	$Q_{n+1}$
0	0	$Q_n$
0	1	0
1	0	1
1	1	$\overline{Q_n}$

You are encouraged to derive this table yourselves.

# Summary

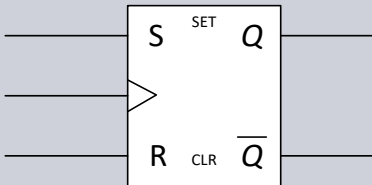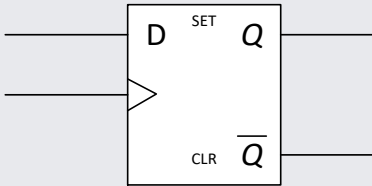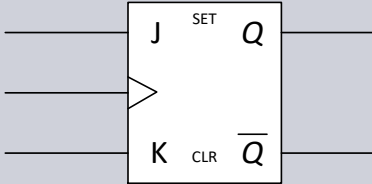Flip-flop	Graphical symbol	Truth table															
S-R		<table><tr><th>S</th><th>R</th><th><math>Q_{n+1}</math></th></tr><tr><td>0</td><td>0</td><td><math>Q_n</math></td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>-</td></tr></table>	S	R	$Q_{n+1}$	0	0	$Q_n$	0	1	0	1	0	1	1	1	-
S	R	$Q_{n+1}$															
0	0	$Q_n$															
0	1	0															
1	0	1															
1	1	-															
D		<table><tr><th>D</th><th><math>Q_{n+1}</math></th></tr><tr><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td></tr></table>	D	$Q_{n+1}$	0	0	1	1									
D	$Q_{n+1}$																
0	0																
1	1																
J-K		<table><tr><th>J</th><th>K</th><th><math>Q_{n+1}</math></th></tr><tr><td>0</td><td>0</td><td><math>Q_n</math></td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td><math>\overline{Q_n}</math></td></tr></table>	J	K	$Q_{n+1}$	0	0	$Q_n$	0	1	0	1	0	1	1	1	$\overline{Q_n}$
J	K	$Q_{n+1}$															
0	0	$Q_n$															
0	1	0															
1	0	1															
1	1	$\overline{Q_n}$															


# Usage example



- Suppose we want to design a 2-bit decremental counter J-K flip flops that repeatedly produces the sequence of output of 3, 2, 1, 0, 3, 2, 1, 0, ...
- Number of flip-flops needed : 2

# Design

Current		Next		Inputs			
$Q_B$	$Q_A$	$Q_B$	$Q_A$	$J_B$	$K_B$	$J_A$	$K_A$
0	0	1	1	1	d	1	d
0	1	0	0	0	d	d	1
1	0	0	1	d	1	1	d
1	1	1	0	d	0	d	1

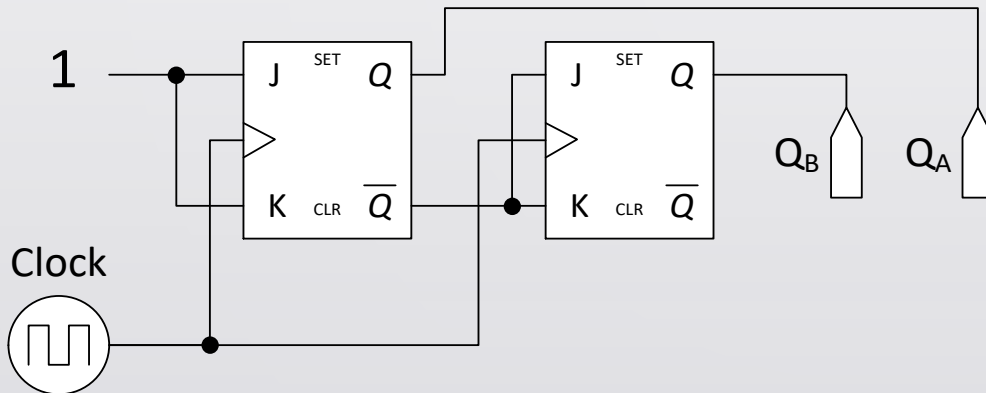

Truth table for  $J_B$ :

	$Q_A$	
	0	1
$Q_B$ 0	1	d
$Q_B$ 1	d	d

$J_B = \overline{Q_A}$

Truth table for  $K_B$ :

	$Q_A$	
	0	1
$Q_B$ 0	d	d
$Q_B$ 1	1	d

$K_B = \overline{Q_A}$

Truth table for  $J_A$ :

	$Q_A$	
	0	1
$Q_B$ 0	1	d
$Q_B$ 1	1	d

$J_A = 1$

Truth table for  $K_A$ :

	$Q_A$	
	0	1
$Q_B$ 0	d	1
$Q_B$ 1	d	1

$K_A = 1$


# Alternative way



Current		Next	
$Q_B$	$Q_A$	$Q_B$	$Q_A$
0	0	1	1
0	1	0	0
1	0	0	1
1	1	1	0
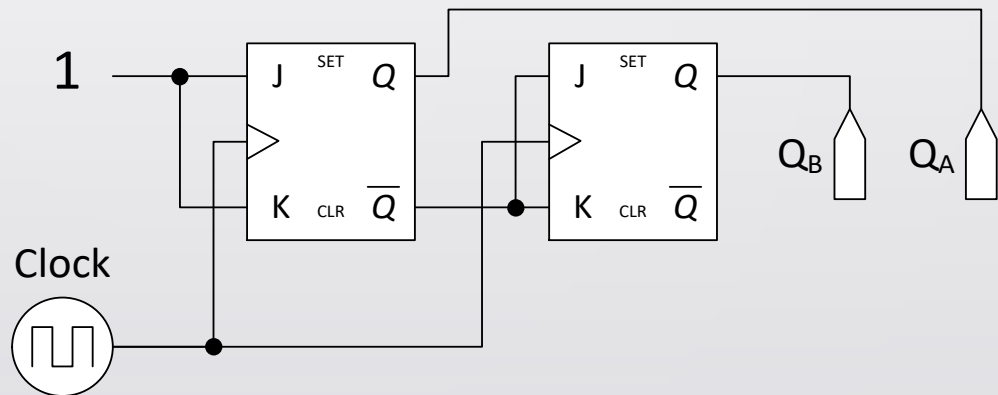
## Observation

$Q_A$  is simply toggling each time  
 $Q_B$  is toggled only when  $Q_A$  is 0




# Exercise



- Expand the previous example to a 3-bit decremental counter.
  - How about 4-bit?

# Solution

Current			Next		
$Q_C$	$Q_B$	$Q_A$	$Q_C$	$Q_B$	$Q_A$
0	0	0	1	1	1
0	0	1	0	0	0
0	1	0	0	0	1
0	1	1	0	1	0
1	0	0	0	1	1
1	0	1	1	0	0
1	1	0	1	0	1
1	1	1	1	1	0

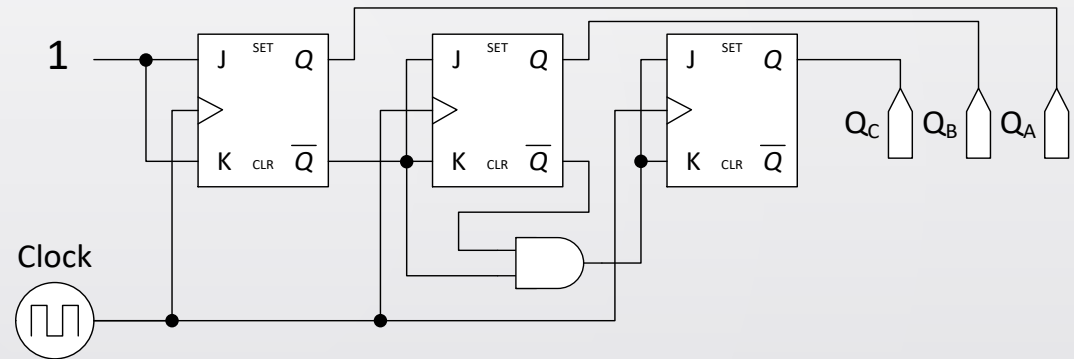



# Solution (4-bit)

